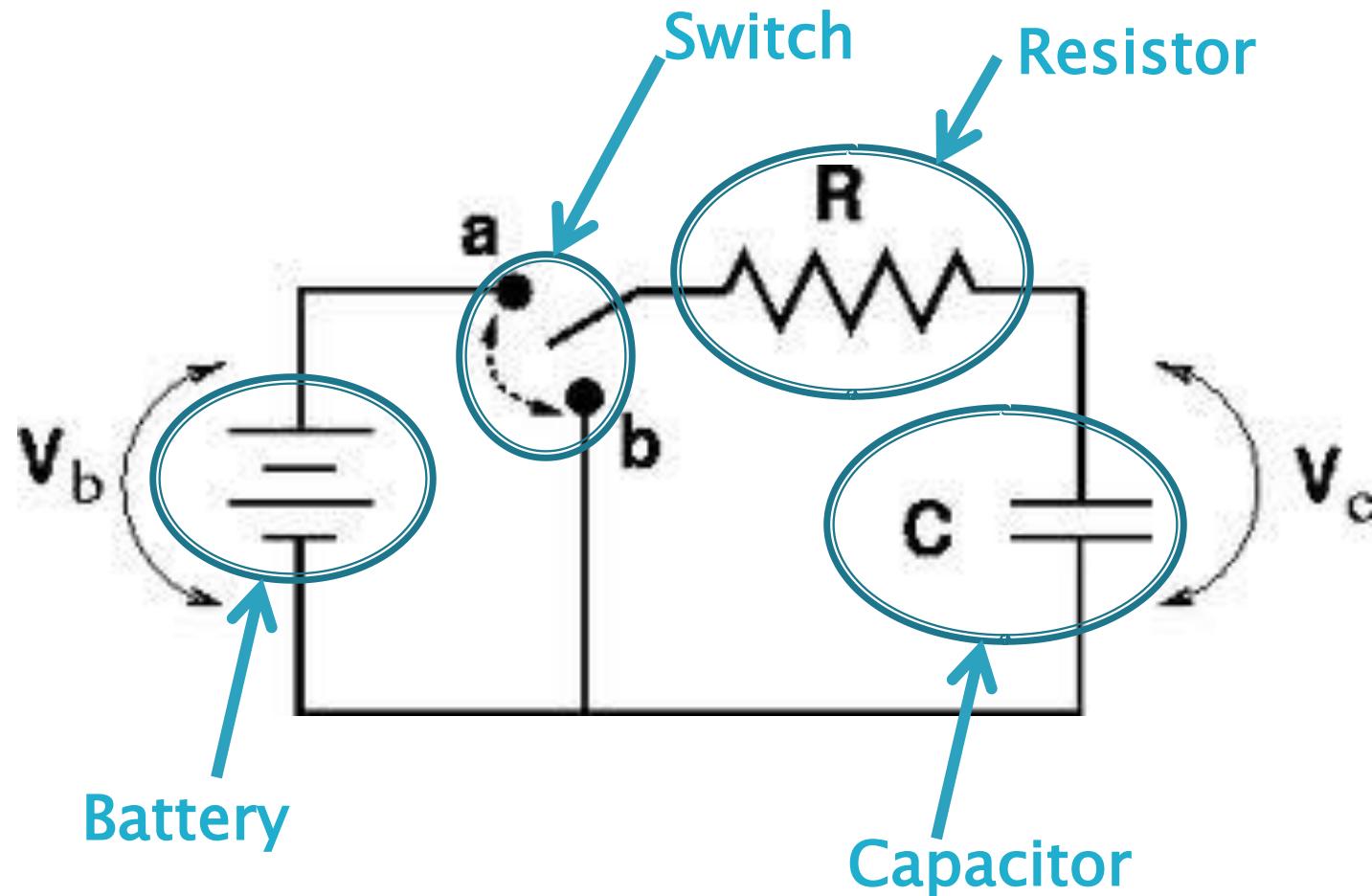


Transient Response of an RC Circuit (Exponential Decay)

Scott Starks, PhD, PE
ECE Department
UTEP


Switched RC Circuit Diagram



Description of the Components


- ▶ V_b : Battery (say, 12 V battery you could buy at the store.)
- ▶ R : Resistor (electrical component that is commonly used to regulate the amount of current that flows in a circuit.)
- ▶ C : Capacitor (electrical component that stores energy in an electric field.)
- ▶ V_c : Voltage across the capacitor

Switch ($t \leq 0$)

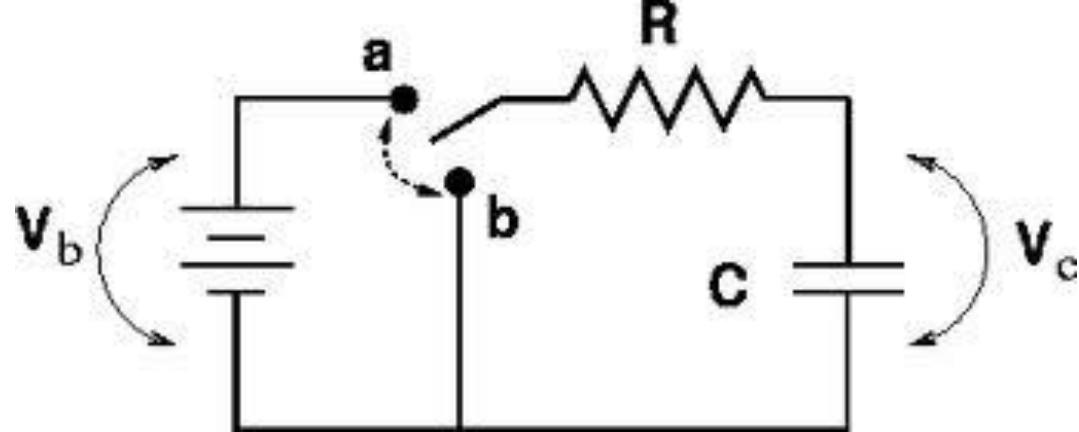

- ▶ Suppose that for time, $t \leq 0$, the switch is at position a.
- ▶ The battery “charges” the capacitor.
- ▶ The value of the capacitor voltage, V_c will be the same as the voltage of the battery, 12 V.

Switch ($t > 0$)

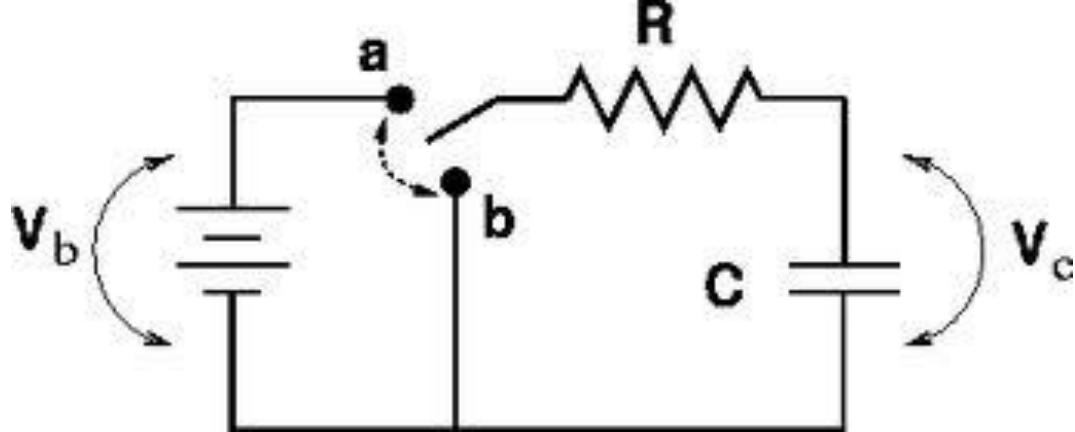


- ▶ Suppose that for time, $t > 0$, the switch is moved instantaneously to position b.
- ▶ The value of the capacitor voltage, V_c , cannot change instantaneously.
- ▶ Instead, the capacitor voltage will “decay exponentially”, according to the formula

$$V_C = V_b e^{-\left(\frac{t}{RC}\right)}$$

Exponential Decay

- ▶ The capacitor voltage will decay from a maximum value of 12 V at time $t = 0$, to a value of 0 as t approaches ∞ .
- ▶ The values of R and C will determine how quickly the decay will occur.
- ▶ The product, $\tau=RC$, is called the “time constant” of the circuit.
- ▶ One may control how quickly the voltage decays by choosing different values for the “time constant”.

Let's Use Actual Values for R and C

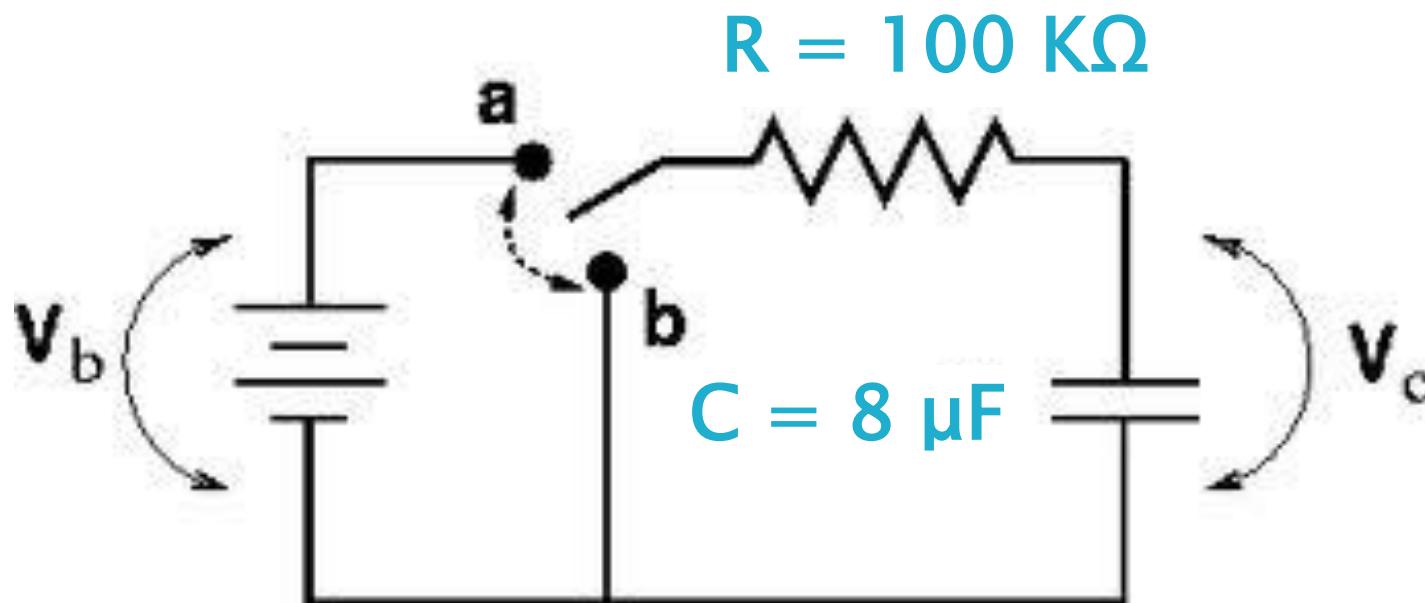

$$R = 100 \text{ k}\Omega = 100 \times 10^3 \Omega$$

$$C = 8 \mu\text{F} = 8 \times 10^{-6} \text{ F}$$

$$\tau = (100 \times 10^3)(8 \times 10^{-6}) = 0.8 \text{ seconds}$$


$$\tau = 800 \text{ ms}$$

Tabular Representation

t	Vc
0	12.00
0.2	9.35
0.4	7.28
0.6	5.67
0.8	4.41
1	3.44
1.2	2.68
1.4	2.09
1.6	1.62
1.8	1.26
2	0.99
2.2	0.77
2.4	0.60
2.6	0.47
2.8	0.36
3	0.28
3.2	0.22
3.4	0.17
3.6	0.13
3.8	0.10
4	0.08

Plot of V_C


V_C (Volts)

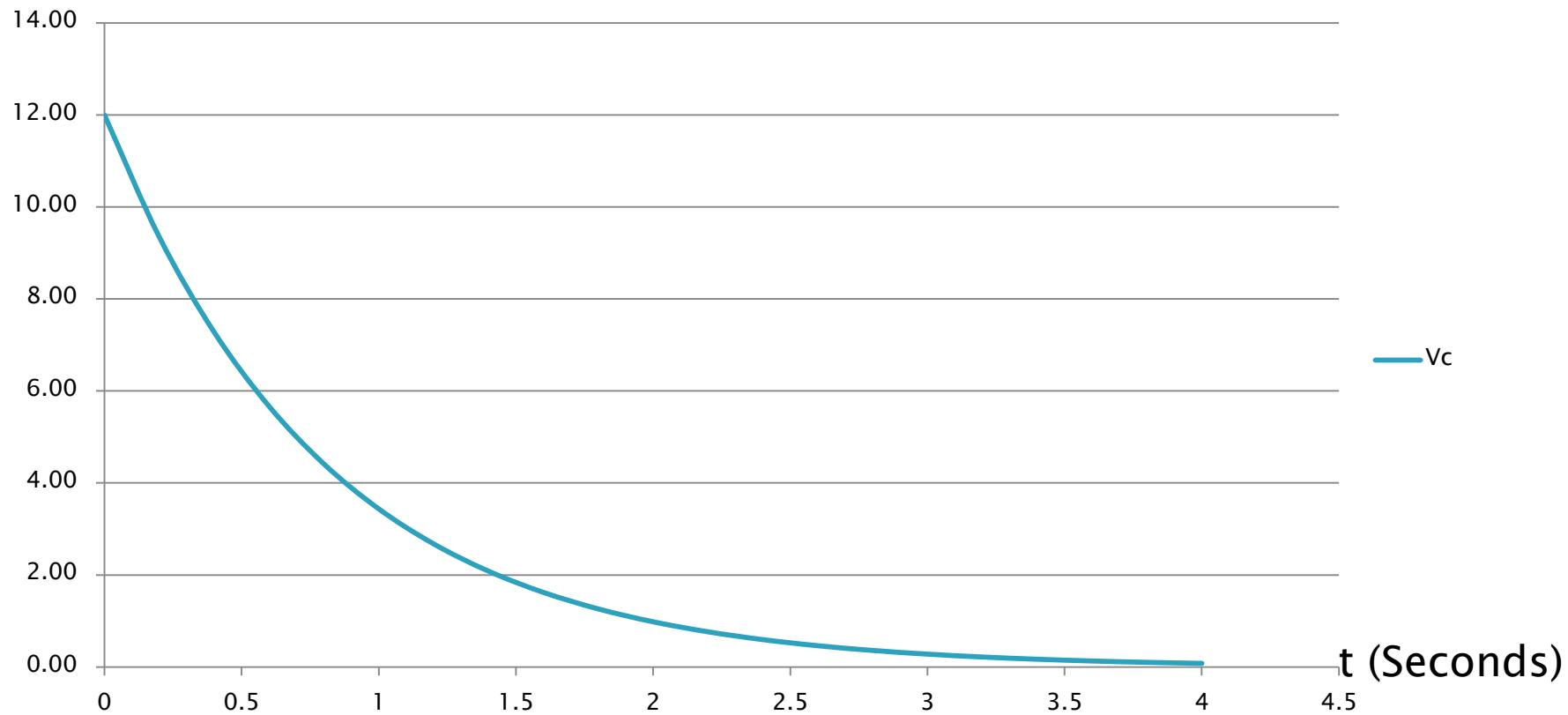

Time Constant

- ▶ We found the value for the time constant for our circuit to be $\tau = 800 \text{ ms}$.
- ▶ The formula for the capacitor voltage is
$$V_C = 12 e^{-(t/RC)} = 12 e^{-(t/\tau)} = 12 e^{-(t/0.8)}$$
- ▶ When $t = \tau = 0.800 \text{ s}$, the capacitor voltage
$$\begin{aligned} V_C &= 12 e^{-(0.800/0.800)} = 12 e^{-1} \\ &= 12(0.368) = 4.41 \text{ V} \end{aligned}$$
- ▶ The time constant tells us **how long** it takes for the voltage to decay to 36.8% of its original value.

Time Constant Shown

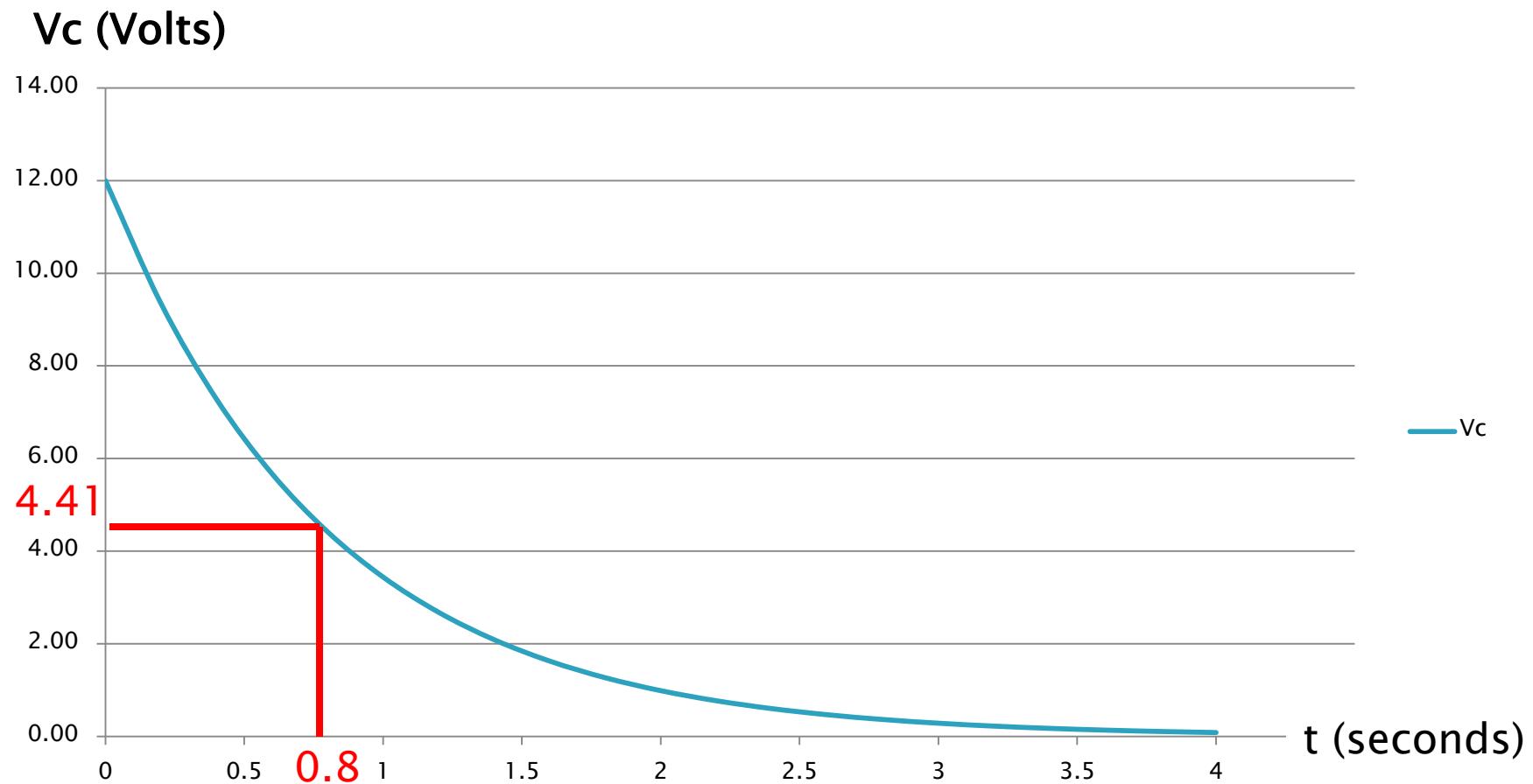

Summary

- ▶ Exponential decay occurs in applications in a variety of fields in science and engineering.
- ▶ We have shown an example taken from physics and electrical engineering, involving the capacitor voltage of a switched RC circuit.
- ▶ One may “control” the rate at which the decay occurs by varying the values of the resistor and the capacitor, thus influencing the time constant of the circuit.