

Consider a switched RC circuit as shown below. Suppose the switch is initially in position a. At time $t = 0$, the switch is instantaneously moved to position b. The initial voltage on the capacitor is the same as that of the battery for all time $t \leq 0$.

Just as was done in the lecture, let's use a 12 V battery and an $8 \mu\text{F}$ capacitor. Let's change the value of the resistor to $200 \text{ k}\Omega$. Answer the following questions.

- What is the value of the time constant (τ) of the circuit?
- Find an expression for the capacitor voltage V_C .
- Sketch a plot of the capacitor voltage as a function of time.
- Compare and contrast this plot to the one that was presented in class.

